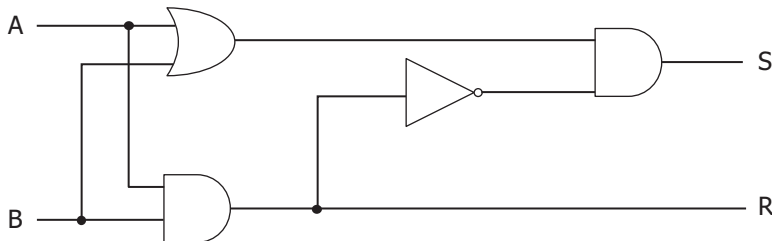


Summary

- Binary addition can be carried out using a half adder or a full adder circuit.
- SR or JK flip-flop circuits can be used to store a bit value.
- There are Boolean algebra laws that can be used to simplify logic expressions.
- The sum-of-products method can be used to create an equivalent logic expression containing minterms from a truth table.
- A Karnaugh map is a representation of a truth table that allows a simplified logic expression to be derived from a truth table.

Exam-style Questions

1 a Consider the following circuit:



- i Identify the **three** different logic gates used. [2]
- ii Complete the following truth table for the circuit for the inputs shown for A and B. [5]

Inputs		Workspace	Outputs	
A	B		S	R
0	0			
0	1			
1	0			
1	1			


b For the circuit shown in **part a**, identify the type of circuit and what the outputs represent. [3]

2 a Consider the following truth table:

A	B	X
0	0	1
0	1	0
1	0	1
1	1	1

- i Using the sum-of-products approach, write a Boolean expression that matches the logic. [3]
- ii For the rows that have $A = 1$, the output for X is 1. Explain how this would be reflected in a simplified form of Boolean expression matching the truth table. [2]

b Consider the following circuit:

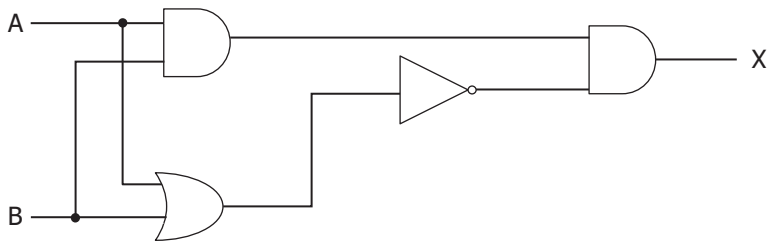

- i** Using your knowledge of the truth table for an AND gate, write a Boolean algebra expression for the output from the first AND gate. [2]
- ii** Using your knowledge of the truth table for an OR gate write a Boolean algebra expression for the output from the OR gate. [3]
- iii** Using De Morgan's law, write the logic expression for the output from the NOT gate. [4]

3 a Consider the following truth table:

A	B	X
0	0	1
0	1	0
1	0	1
1	1	1

- i** Sketch a Karnaugh map to match this truth table. [4]
- ii** Use the Karnaugh map to write a Boolean algebra expression for this logic. [3]

b Consider the truth table shown in **part a**.

- i** Use the sum-of-products method to write a Boolean algebra expression from the truth table. [3]
- ii** Use Boolean algebra to demonstrate that this expression can be simplified to give the same expression created from the Karnaugh map. Hint: you might wish to use the fact that

$$A \cdot \bar{B} = A \cdot \bar{B} + A \cdot B$$


4 a Complete the truth table for this NAND gate:

```
graph LR; A((A)) --- NAND[NAND]; B((B)) --- NAND; NAND --- X((X))
```

A	B	X
0	0	
0	1	
1	0	
1	1	

[1]

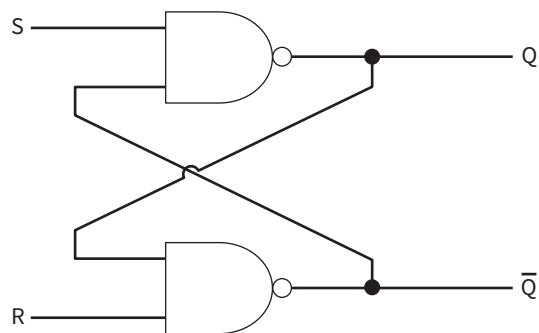An SR flip-flop is constructed using two NAND gates.



b i Complete the truth table for the SR flip-flop.

	S	R	Q	\bar{Q}
Initially	1	0	0	1
R change to 1	1	1		
S changed to 0	0	1		
S changed to 1	1	1		
S and R changed to 0	0	0		

[4]

ii One of the combinations in the truth table should not be allowed to occur.
State the values of S and R that should not be allowed. Justify your choice.

[3]

Another type of flip-flop is the JK flip-flop.

c i Give **one** extra input present in the JK flip-flop.

[1]

ii Give **one** advantage of the JK flip-flop.

[1]

d Describe the role of flip-flops in a computer.

[2]


Cambridge international AS & A Level Computer Science 9608 paper 31 Q5 June 2016

5 a i A half adder is a logic circuit with the following truth table.

Input		Output	
X	Y	A	B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

365

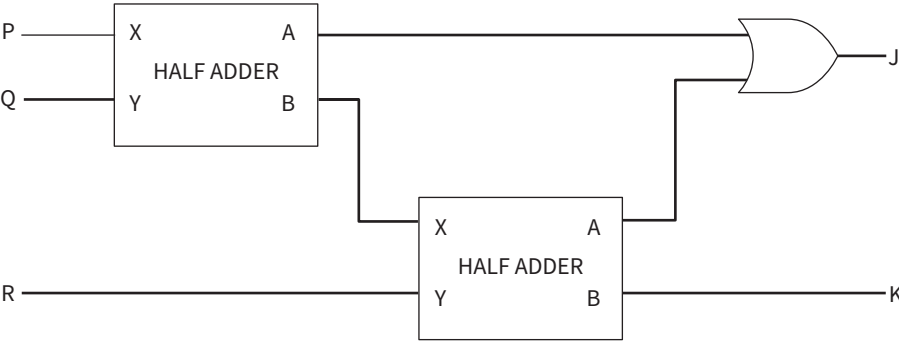The following logic circuit is constructed.



Complete the following truth table for this logic circuit.

Input			Working space		Output	
P	Q	R			J	K
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				


[2]

ii State the name given to this logic circuit. [1]

iii Name the labels usually given to **J** and **K**.

Explain why your answers are appropriate labels for these outputs. [4]

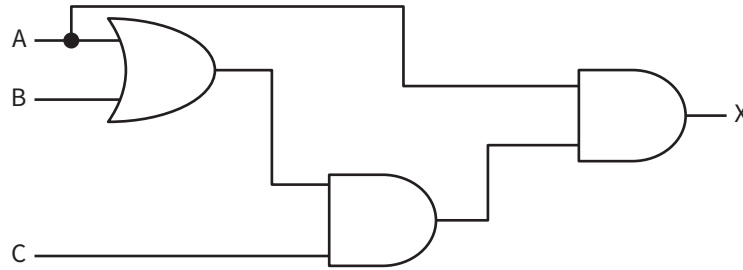b i Write down the Boolean expression corresponding to the following logic circuit:



ii Use Boolean algebra to simplify the expression given in **part b(i)**.

Show your working. [4]

Cambridge International AS & A Level Computer Science 9608 Paper 32 Q5 November 2016