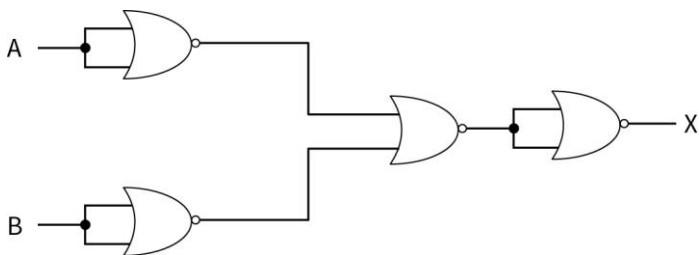



# Worksheet 19.1: for testing basic understanding

- 1 A logic circuit can be described as combinational or sequential.
- a Explain the difference between the two types of circuit.
  - b Are there any differences in the components used for the two types?
  - c Give an example for each type.
- 2 a Create a truth table for the following circuit:



- b What is the overall logic equivalent to?
  - c Why are circuits often constructed from NOR gates?
  - d Why would this logic be created using NOR gates?
- 3 Choose whether each statement is true or false:
- A A half adder circuit has two inputs and two outputs.
  - B A full adder circuit has three inputs and three outputs.
  - C A full adder is an example of a sequential circuit.
  - D A clocked circuit has an extra input.
  - E A half adder circuit can be constructed from only NAND gates and a full adder circuit can be constructed from only NOR gates.
- 4 Match each symbol (only partially labelled) with the correct identification.

	Half adder
	Full adder
	SR flip-flop
	JK flip-flop

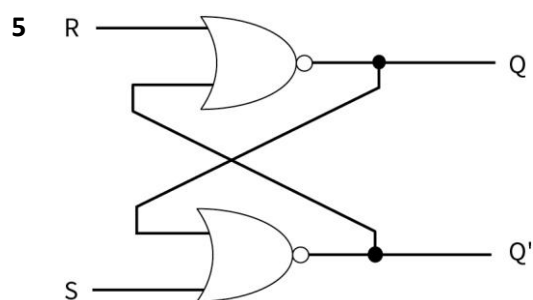

The above diagram shows a logic circuit for an RS flip-flop. The table below shows some relevant rows of the corresponding truth table. Each row of the table is labelled A–H.

	Input signals		Initial state		Final state	
	S	R	Q	Q'	Q	Q'
A	1	0	0	0	1	0
B	0	1	0	0	0	1
C	0	0	1	0	1	0
D	0	0	0	1	0	1
E	1	0	0	1	1	0
F	1	0	1	0	1	0
G	0	1	0	1	0	1
H	0	1	1	0	0	1

Identify a row that shows:

- that the flip-flop retains the value stored if no input signal is received
  - how an undefined state can be set to a state in which a value is stored
  - no change even though a signal is input
  - a value being changed but where there must have been an intermediate state (as demonstrated by examination of the circuit diagram).
- 6 Starting with the expression  $\bar{A}.B + A.\bar{B} + A.B$ , show the sequence of steps from the following list that can be used to convert this to the simplest possible form:
- $\bar{A}.B + A.\bar{B} + A.B$
  - $A + B$
  - $\bar{A}.B + A.\bar{B} + A.B + A.B$
  - $A.1 + 1.B$
  - $A.(B + \bar{B}) + (A + \bar{A}).B$

7 Consider the following truth table:

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

a Create the corresponding Karnaugh map.

b Create the Boolean algebra expression corresponding to this Karnaugh map.

8 Match each Karnaugh map with the corresponding Boolean algebra expression.

BC A	00	01	11	10
0	1	1	1	1
1	0	0	0	0

BC A	00	01	11	10
0	0	1	1	1
1	0	1	1	1

BC A	00	01	11	10
0	1	1	1	0
1	0	1	1	1

BC A	00	01	11	10
0	1	0	1	1
1	1	0	1	1

$$B + \bar{C}$$

$$\bar{A}.\bar{B} + C + A.B$$

$$\bar{A}$$

$$B + C$$